

Experiment 4: Applications of KMap method.

Objective:

- To investigate the rules of kmap.
- To gain experience working with ~~per~~ practical circuits.
- To simplify a complex function using kmap.

Required equipments:

- AND gate
- OR gate
- Not gate
- LOGIC STATE
- LOGIC PROBE

Function:

$$i) F(A, B, C, D) = \sum (1, 3, 9, 10, 13, 15)$$

$$ii) F(A, B, C, D) = \sum (1, 4, 10, 15) + d(3, 5, 13, 14)$$

$$i) F(A, B, C, D) = \sum (0001, 0011, 1001, 1010, 1101, 1111)$$

$$ii) F(A, B, C, D) = \sum (0001, 0100, 1010, 1111) + d(0011, 0101, 1101, 1110)$$

~~Experimental setup~~ Simplify: not a good idea

1) $F(A, B, C, D) = \sum (1, 3, 9, 10, 13, 15)$

~~$F(A, B, C, D) = A'B'D$~~

	$c'd'$	$c'd$	cd	cd'
$A'B'$	0	1	1	3
$A'B$	4	5	7	6
AB	12	13	15	14
AB'	8	9	11	10


$\rightarrow A'B'D$
 $\rightarrow ABD$
 $\rightarrow AB'CD'$
 $\rightarrow AC'D$

2) $F(A, B, C, D) = \sum (1, 4, 10, 15) + d(3, 5, 13, 14)$


	$c'd'$	$c'd$	cd	cd'
$A'B'$	0	1	3	2
$A'B$	4	5	7	6
AB	12	13	15	14
AB'	8	9	11	10

$\rightarrow A'B'D$
 $\rightarrow A'BC'$
 $\rightarrow ACD'$
 $\rightarrow ABD$

Experimental setup: For a function (1)

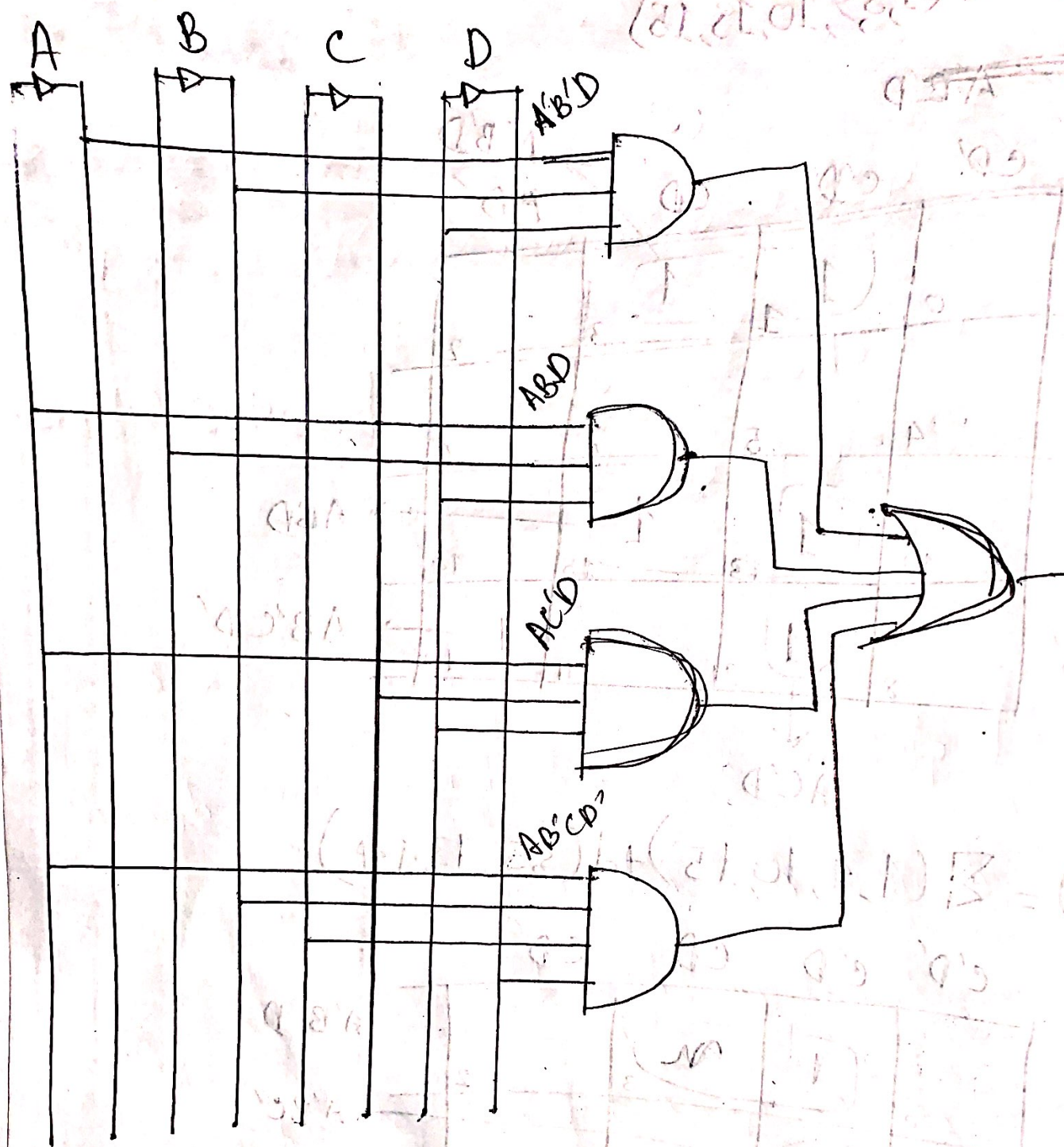

For function (2)

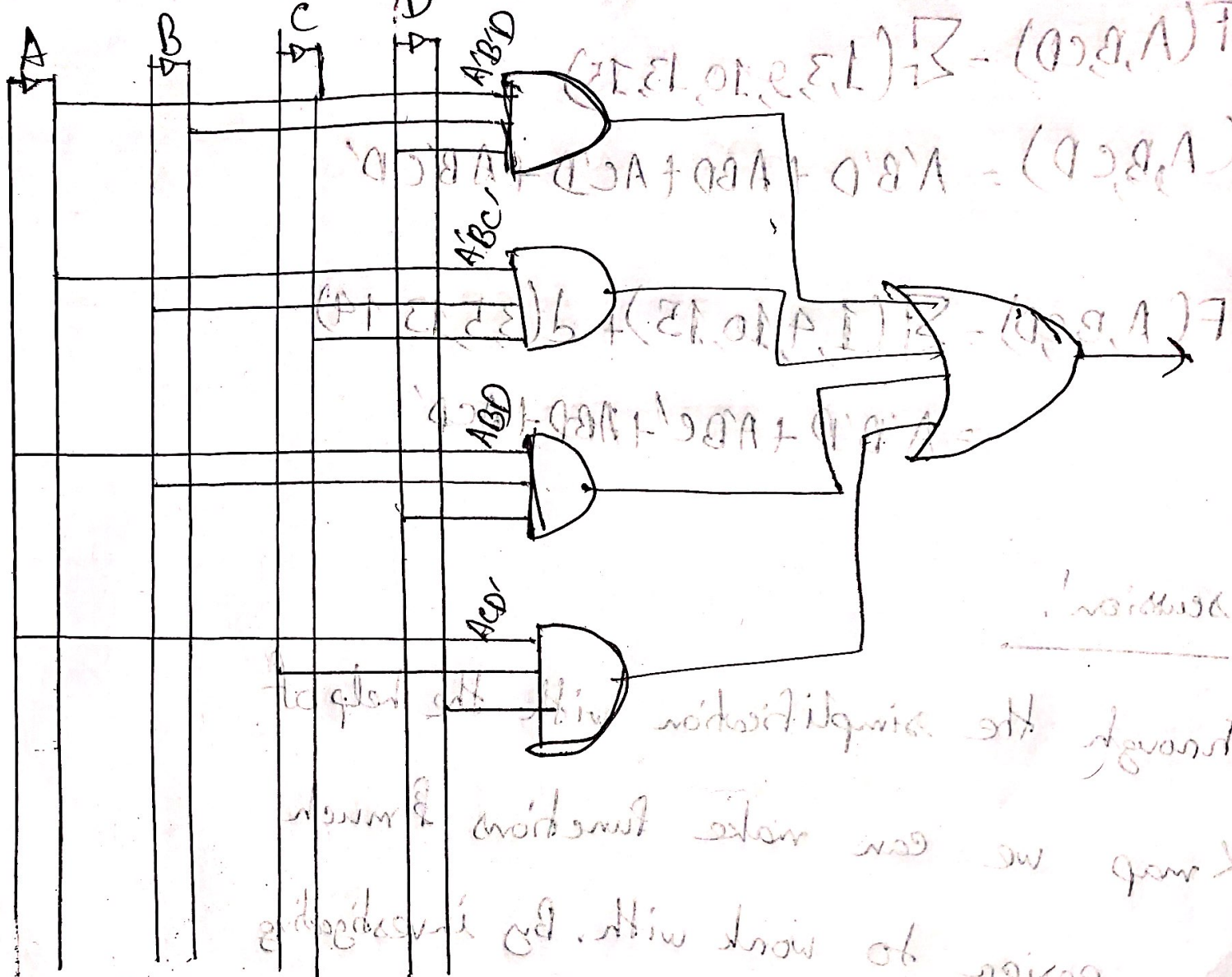

Result!

~~The~~ The output of functions from Kmap are

$$1) F(A, B, C, D) = \sum (1, 3, 9, 10, 13, 15)$$

$$F(A, B, C, D) = A'B'D + ABD + AC'D + AB'CD'$$

$$2) F(A, B, C, D) = \sum (1, 4, 10, 15) + \sum (3, 5, 13, 14)$$

$$= A'B'D + AB'CD + ABD + AC'D'$$

Discussion!

Through the simplification with the help of

Kmap we can make functions so much more easier to work with. By investigating

~~through~~ with the rule of Kmap we can

simplify any complex function.