

CSE260 Lab Report

**Experiment Name: Familiarization of
fundamental logic gates.**

Submitted by

Name: Khaled Mushahed Hossain

ID: 20101297

Section: 09

Date: 04/03/2021

Name of experiment.

Familiarization of fundamental logic gates.

Object:





- To get familiarised with fundamental logic gates and demonstrate the input output relationship of 1, 2-input AND (IC-7408), OR (IC-7432) and NOT (IC-7404) gates by constructing their truth table.
- To get familiarized with other logic gates like NAND (IC-7400), NOR (IC-7402), XOR (IC-7486) and XNOR (IC-74266).


Required components:

- | | |
|--------|----------------|
| * AND | * LOGIC STATE |
| * OR | * LOGIC PROBE |
| * NOT | * LED - BLUE |
| * NOR | * LED - GREEN |
| * NAND | * LED - ORANGE |
| * XOR | * LED - PINK |


- * LED - PURPLE
- * LED - YELLOW
- * LED - RED.

Experimental Setup

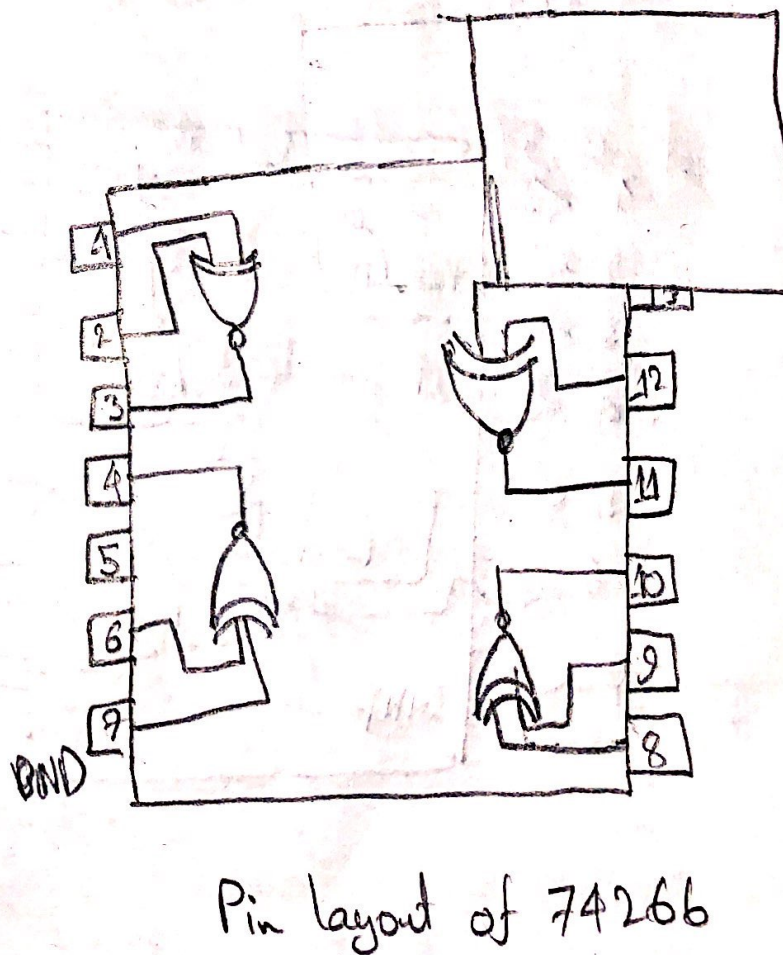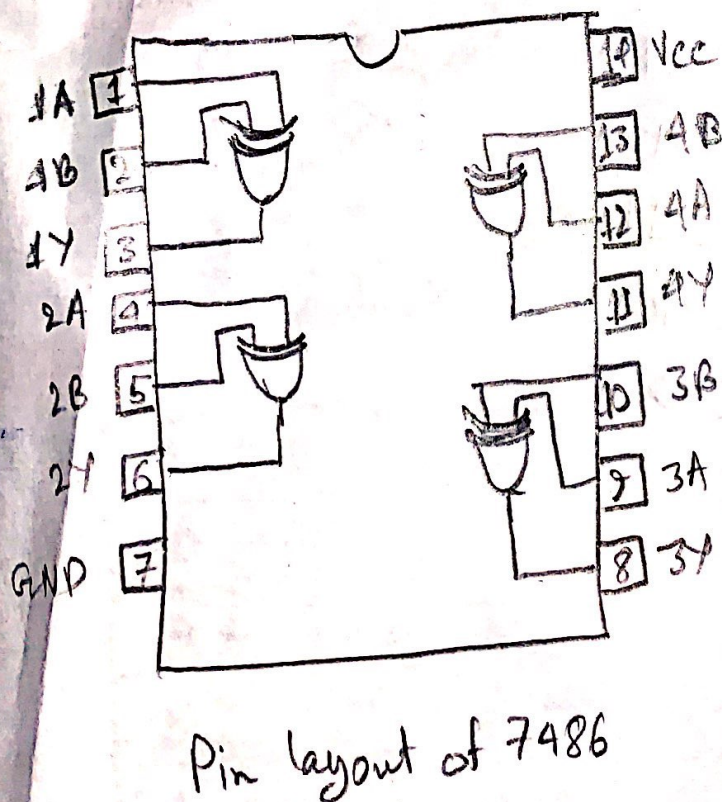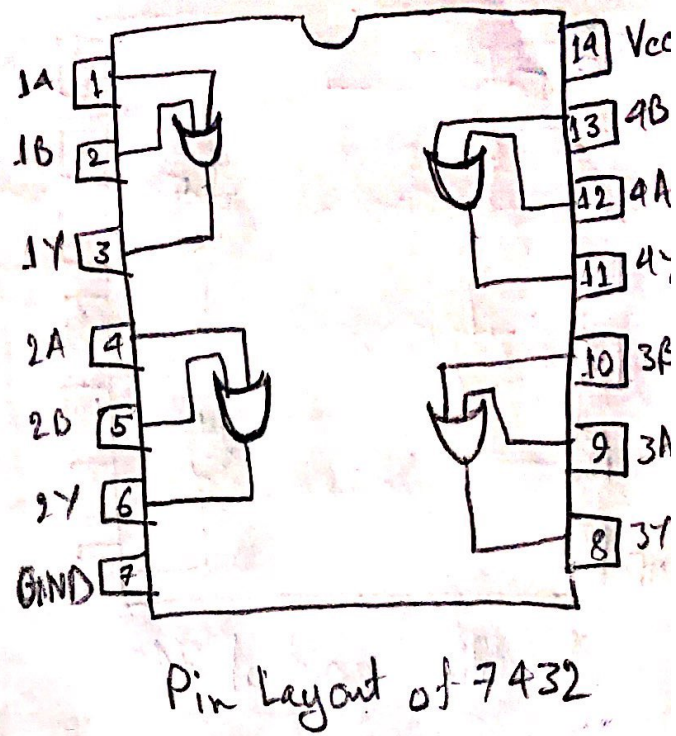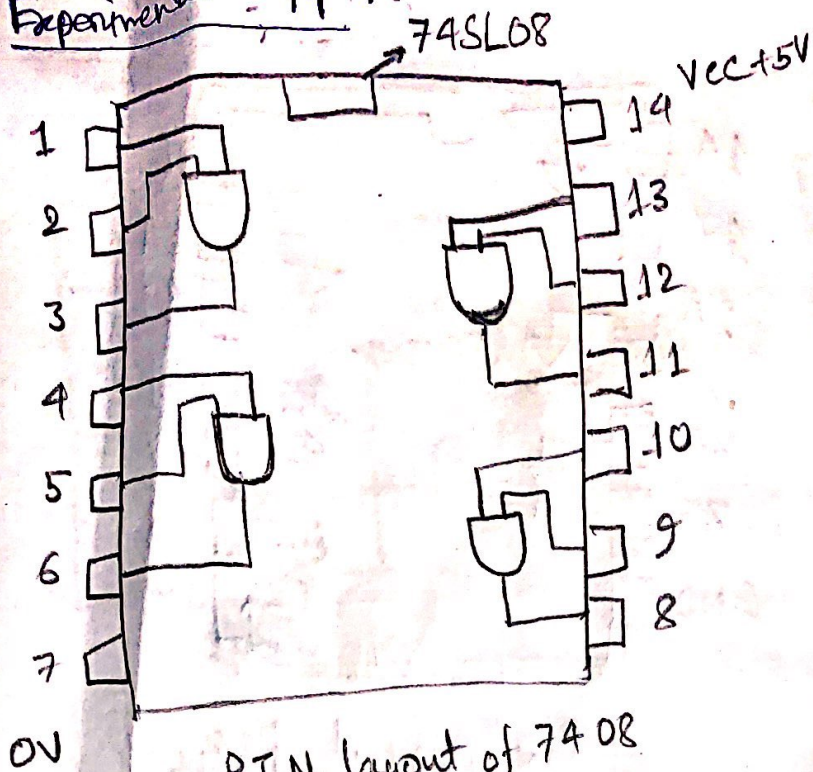


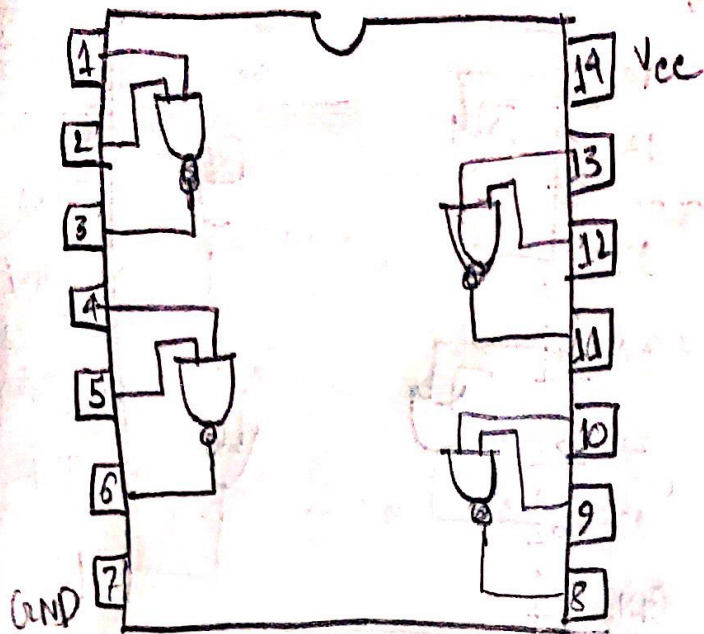

Pin layout of 7400

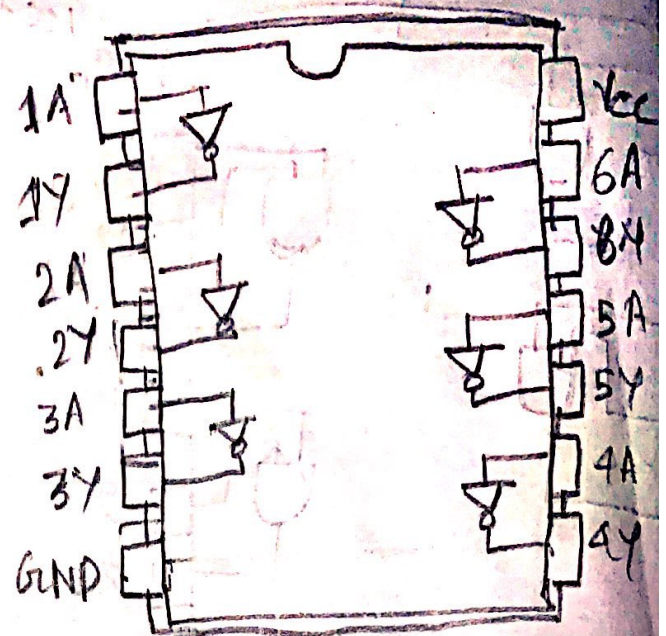

Pin layout of 7401

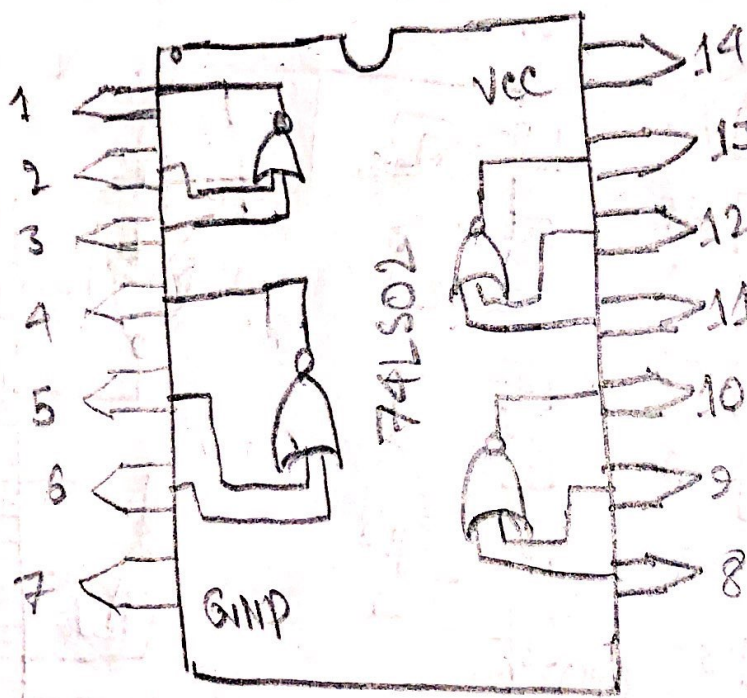

Result / Truth Table :

A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1

AND

A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

OR

A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

NAND

A	B	$\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

XOR

A	B	$\overline{A \oplus B}$
0	0	1
0	1	0
1	0	0
1	1	1

XNOR

A	\overline{A}
0	1
1	0

NOT

Discussion:

By observing the truth table we can see that, every gate needs two inputs except NOT which needs only one input.

NAND gate is the combination of AND gate and NOT gate and NOR gate is the combination of OR gate and NOT gate and XOR gate is the combination of OR gate and NOT gate combine to turn into XNOR gate.

A	NOT A
0	1
1	0

A	B	A AND B
0	0	0
0	1	0
1	0	0
1	1	1

A	B	A OR B
0	0	0
0	1	1
1	0	1
1	1	1

XNOR