

## Experiment No. 6: Implementation of 4 bit Magnitude Comparator


### Objectives:

- Drawing the circuit that will act as a Magnitude Comparator.  
Your circuit should be able to compare two 4 bit numbers.
- To implement my circuit (for two 4-bit numbers).

### Required Equipments:

- AND gate
- NOT gate
- NOR gate
- LOGIC PROBE
- LOGIC STATE.
- OR Gate
- 4072
- 4082
- 7411

# Experimental Setup:-

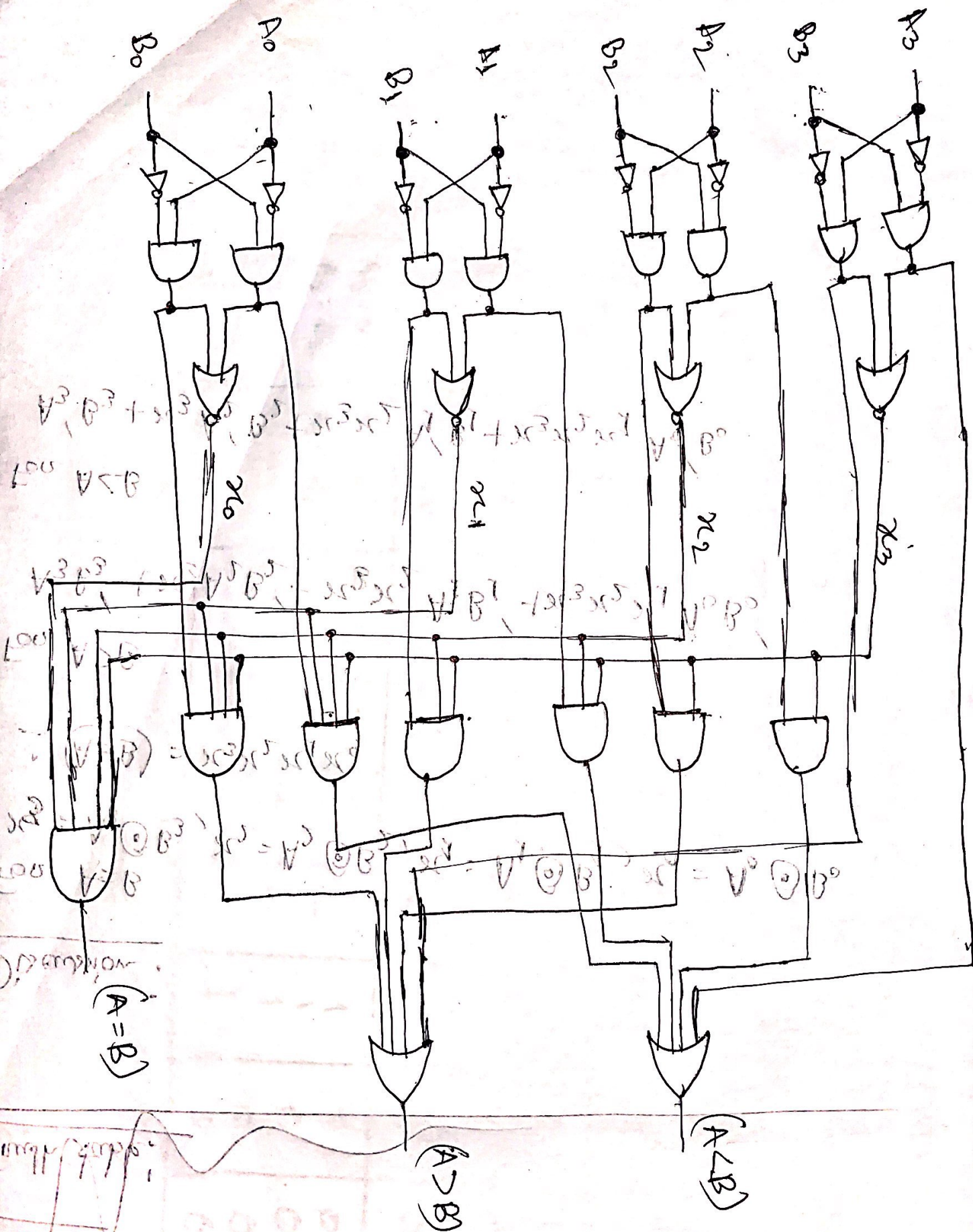



# Truth Table:

Compare				Inputs			Outputs		
				Compare					
$A_3 B_3$	$A_2, B_2$	$A_1, B_1$	$A_0, B_0$	$A < B$	$A = B$	$A > B$	$A < B$	$A = B$	$A > B$
$A_3 > B_3$	—	—	—	—	—	—	0	0	1
$A_3 = B_3$	$A_2 > B_2$	—	—	—	—	—	0	0	1
$A_3 = B_3$	$A_2 = B_2$	$A_1 > B_1$	—	—	—	—	0	0	1
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 > B_0$	—	—	—	0	0	1
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	0	0	1	0	0	1
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	0	1	—	0	1	0
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	1	0	—	1	0	0
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 < B_0$	1	—	—	1	0	0
$A_3 = B_3$	$A_2 = B_2$	$A_1 < B_1$	—	—	—	—	1	0	0
$A_3 = B_3$	$A_2 < B_2$	—	—	—	—	—	1	0	0
$A_3 < B_3$	—	—	—	—	—	—	1	0	0

## Discussion :

For  $A=B$

$$\pi_3 = A_3 \odot B_3, \pi_2 = A_2 \odot B_2, \pi_1 = A_1 \odot B_1, \pi_0 = A_0 \odot B_0$$

$$\therefore (A=B) = \pi_3 \pi_2 \pi_1 \pi_0$$

For  $A > B$

$$A_3 B_3' + \pi_3 A_2 B_2' + \pi_3 \pi_2 A_1 B_1' + \pi_3 \pi_2 \pi_1 A_0 B_0'$$

For  $A < B$

$$A_3' B_3 + \pi_3 A_2' B_2 + \pi_3 \pi_2 A_1' B_1 + \pi_3 \pi_2 \pi_1 A_0' B_0$$

