

Experiment-3

Parity Generator (and Checker)

Objective:


- To design and implement an even parity Generator and Even parity checker using XOR gates) (IC-7486)

Required Components and Equipments:


- XOR gate
- LOGIC STATE
- LOGIC PROBE

Diagram of Circuit :

Even Parity generator.

 

Even Parity Checker.

 

Results in Tabulated form:

P_0	D_1	D_2	D_3	Parity bit
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

~~Description~~

Discussion:

The parity rule is that the even parity ~~rule~~ is when we have even number of 1 in our function then we have to determine 0 as a parity bit. But odd number of 1 in ~~the~~ a function the 1 is the parity bit.

- a) 0111; here, there are ^{odd} ~~even~~ number of '1'
so parity bit is '1'
- b) 1001; here, there are even number of '1'
so parity bit is '0'
- c) 0000; ~~here~~ this is even so parity bit is '0'
- d) 0100; odd number of '1' so parity bit is '1'

In the checker is the output is True or '1'
then there will be no error; if it prints
False or '0' then there will be no error.